

## Battery Eliminator Using Zener Diode - Calculations

### 1. Transformer Output:

- Input: 230V AC
- Output (RMS): 9V
- Peak Voltage:  $9 \times 1.414 = 12.7V$

### 2. After Bridge Rectifier:

- Diode drop: 1.4V ( $0.7V \times 2$ )
- DC Voltage:  $12.7V - 1.4V = 11.3V$

### 3. Zener Regulation:

- Zener Voltage: 5V
- Resistor: 1k ohm
- Voltage across R:  $11.3V - 5V = 6.3V$
- Current:  $6.3V / 1k \text{ ohm} = 6.3mA$

### 4. Ripple Voltage:

- $I = 6.3mA$ ,  $C = 100\mu F$ ,  $f = 100Hz$
- $V_r = I / (f \times C) = 0.63V$

### 5. Power Dissipation:

- Resistor:  $P = I^2 \times R = 0.04W$
- Zener:  $P = V \times I = 5V \times 6.3mA = 0.0315W$

Output voltage observed: ~5.7V DC (stable for small devices)